



## Application Details:

In this example RSENSE is set to 20mΩ, giving the nominal 10 Amps output current. To obtain 25 Amps,  $V_{ref}$  would need to be increased to 500mV. This could be done by externally adjusting the voltage to the Soft Start pin. Note that only voltages less than or equal to 0.8 volts can be used. The Soft Start pin has been configured so that voltages above 0.8 volts will not increase the internal reference voltage, it can only be lowered. Voltages below 200mV are not recommended. If a lower voltage is required to reduce power dissipation in the sense resistors, a scaling circuit can be used as was done in Design Solution #33.

<http://www.sipex.com/files/DesignSolutions/Design%20Solution%2033%20SP7652LED%20driver%20w%20dimmer.pdf>


The circuit was also configured to allow dimming of the LED by pulse width modulating the UVIN pin or the VFB pin. By modulating the UVIN pin, slightly better efficiencies are seen at low duty cycles. This is due to the different way each configuration operates. When using the VFB pin, the output is pulled to ground during each cycle. When using the UVIN pin, the converter is simply shut off during each cycle -- this causes the output voltage to drop only to below the LED forward voltage. The next time the converter turns on the output does not have need to rise the full voltage range. Waveforms have been included to illustrate this effect.

## Bill of Materials

Line	Qty	Reference	Manufacturer	Part Description
1	1	U1	Sipex	SP6133
2	3	C1,C2	Murata	22uF, 25V, X5R, 1210
3	1	DBST	Vishay	MBR0530
4	16	LED	Luxeon	Luxeon: LXH LMW1D
5	1	L1	Wurth	7443551130
6	3	M1B,M2T,M2B	NXP (Phillips)	30V, 2.3mΩ, PH3330L
7	4	Ra,b,c,d	Panasonic	20mW, 2512, 1W, 1%, ERJ-M1WSF20MU
8	2	CBST,CF1	Murata	0.1uF
9	1	CSS	Murata	10nF
10	1	CVCC	Murata	10uF
11	1	RSS2	Panasonic	10k
12	1	RSS3	Panasonic	420
13	1	R10	Panasonic	3 Ohm

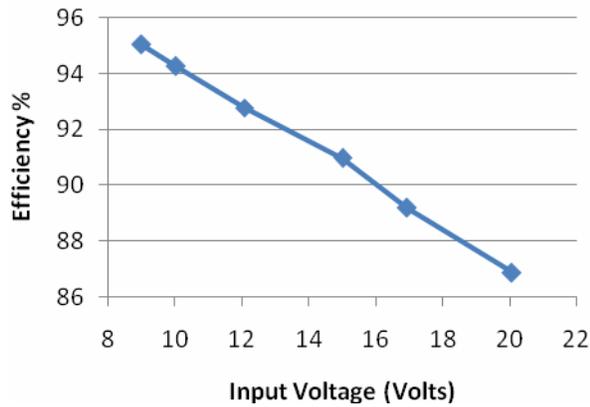
## Results: Converter Efficiency

6133 LED Driver Efficiency over Line - 10Amps




V <sub>IN</sub>	Efficiency
9	95
10	94
12	93
15	91
17	89
20	87

100Hz Strobe - Converter Efficiency

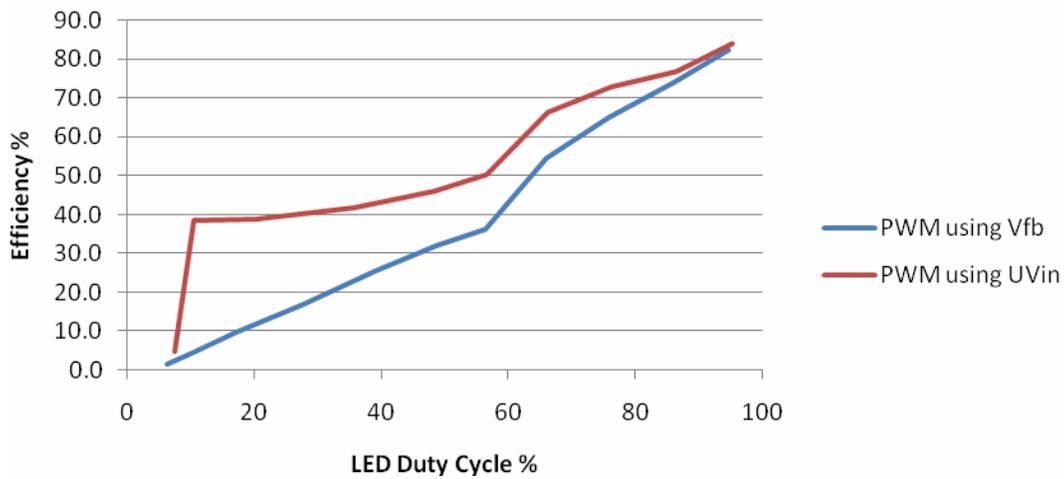


1kHz Strobe - Converter Efficiency

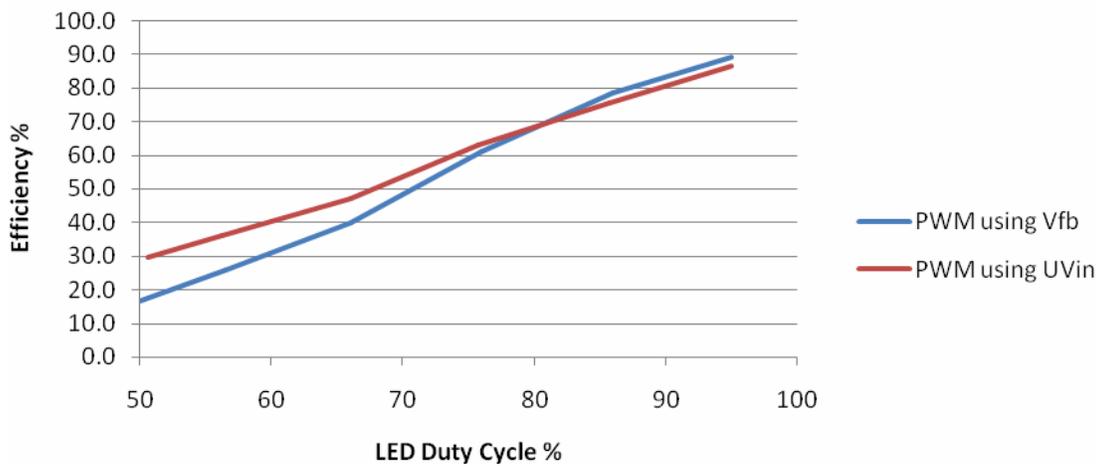


## Results: PWM Strobe Linearity


### 1kHz PWM Duty Cycle Linearity

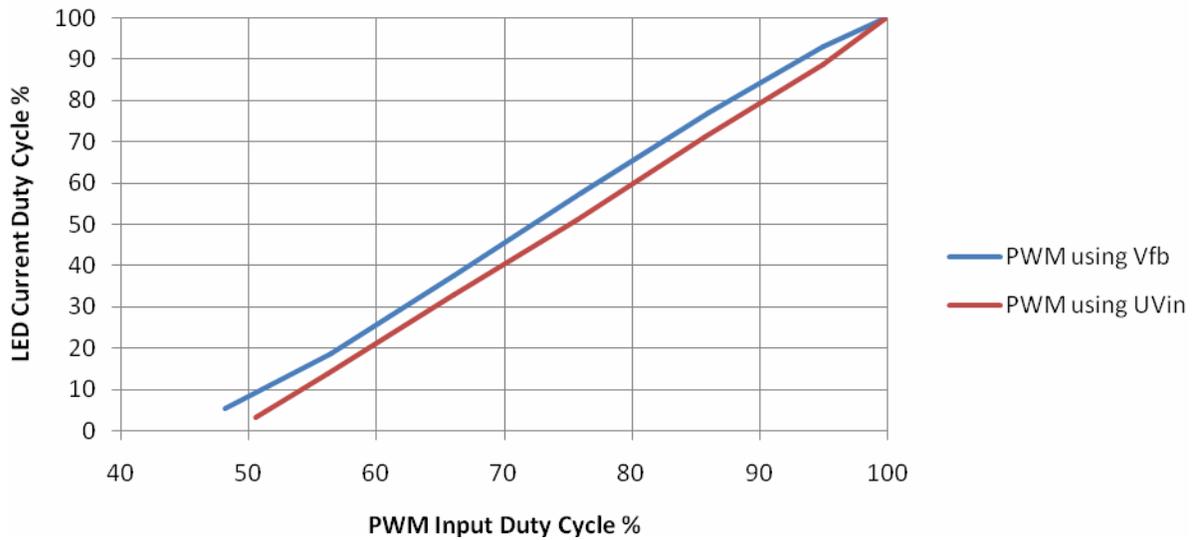

### 100Hz PWM Duty Cycle Linearity

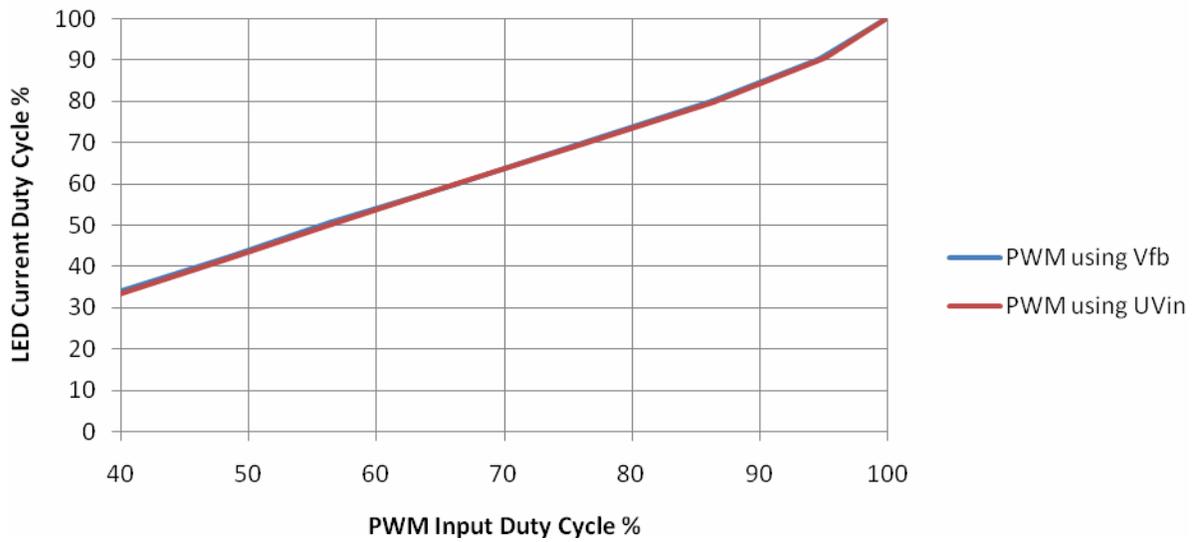


## Waveforms:

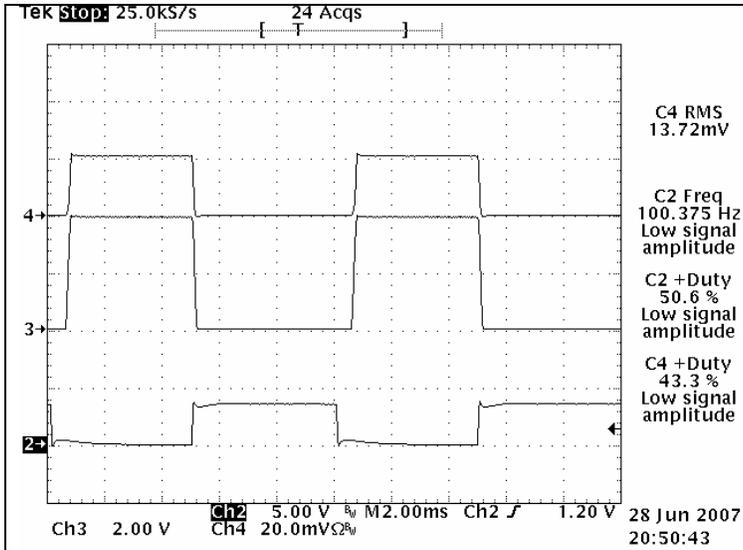

Waveform 1

CH4:  $I_{LED}$  10A/div  
 CH3: VOUT  
 CH2: VFB

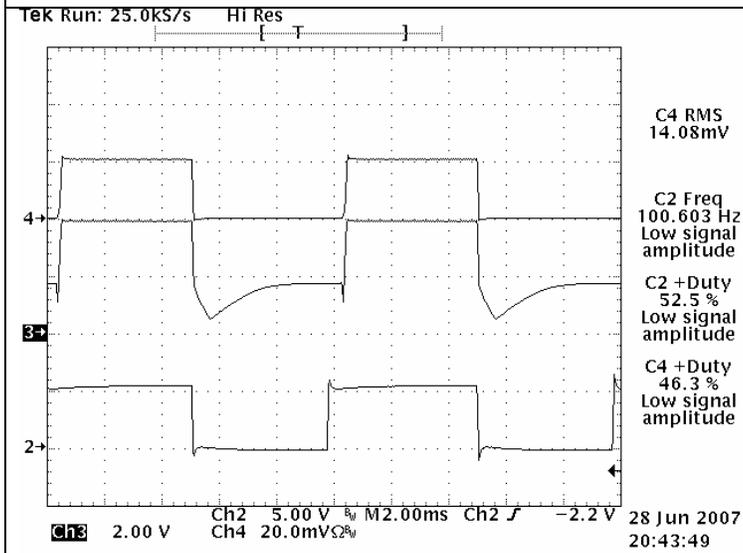


Waveform 2

CH4:  $I_{LED}$  10A/div  
 CH3: VOUT  
 CH2: UVIN

Note the difference in output voltage. When using UVIN the output voltage is not pulled to ground.

### Circuit Schematic

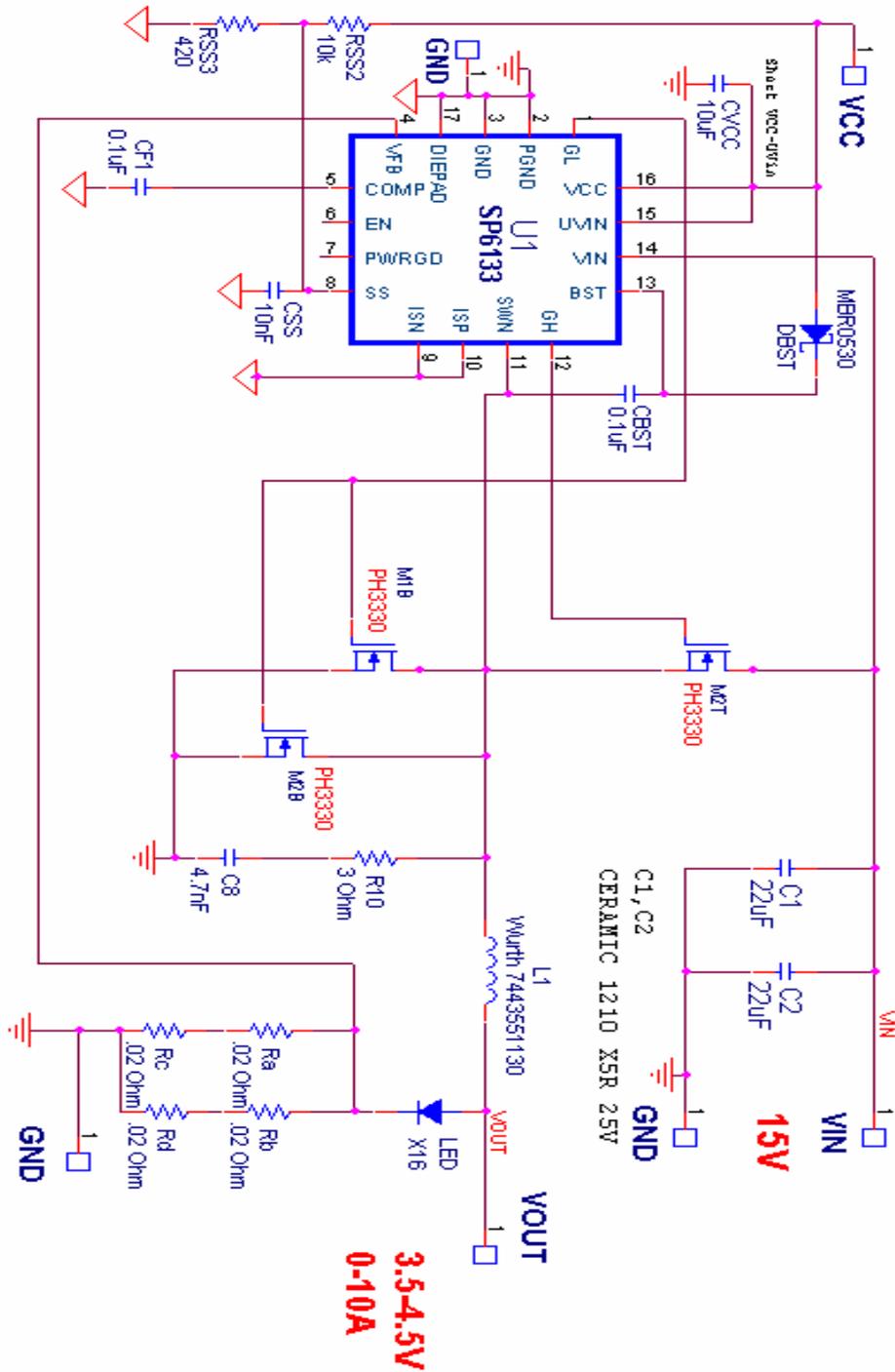

All resistance values are in Ohms.

For further assistance:

Email: [Sipexsupport@sipex.com](mailto:Sipexsupport@sipex.com)  
WWW Support page: <http://www.sipex.com/content.aspx?p=support>  
Live Technical Chat: <http://www.geolink-group.com/sipex/>  
Sipex Application Notes: <http://www.sipex.com/applicationNotes.aspx>



## Sipex Corporation

Headquarters and  
Sales Office  
233 South Hillview Drive  
Milpitas, CA95035  
tel: (408) 934-7500  
faX: (408) 935-7600

Sipex Corporation reserves the right to make changes to any products described herein. Sipex does not assume any liability arising out of the application or use of any product or circuit described herein; neither does it convey any license under its patent rights nor the rights of others.