# **APPLICATION NOTE ANI1**




# 1.8V RS232 Interface Using SP3203E & SP6661

## Introduction

The SP3203E low-power RS232 transceiver operates from a  $V_{CC}$  supplies ranging from 2.7V to 5.5V. It can safely interface to CMOS logic levels between 1.65V and 5.5V by using a logic-level supply voltage on the SP3203E's  $V_L$  pin. The following application example shows a method for generating  $V_{CC}$  from a 1.8V supply for pure 1.8V operation.

1.8V RS-232 apps circuit

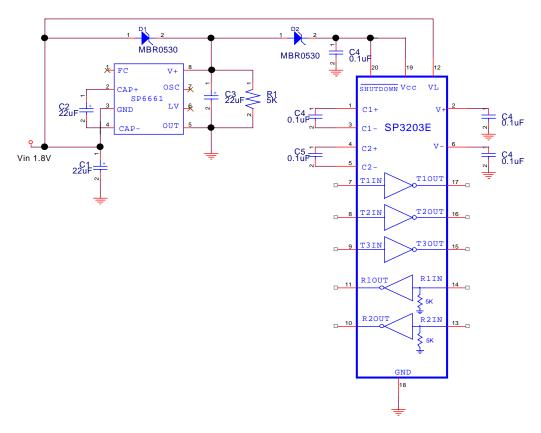

SP6661 Vout test condition.
All TX loaded 3K and Switching at "fin"

Vin	Icc	Vout	fin
1.8	26mA	3.26	
	52mA	3.14	125HZ
1.7	27mA	3.03	0
1.7	47mA	2.94	125HZ

### Notes

D1 is used to help SP66611 start up under load

D2 is used to block unwanted voltage present at Vcc (SP3203) during power off with TTL signals at Txin.

R1 is used to discharge SP6661 Cout during power off for proper start up

(If SP6661 Vout is 200mV or > device will not start)

### For further assistance:

Email: Sipexsupport@sipex.com

WWW Support page: http://www.sipex.com/content.aspx?p=support

Live Technical Chat: http://www.geolink-group.com/sipex/

Sipex Application Notes: http://www.sipex.com/applicationNotes.aspx



Sipex Corporation
Headquarters and
Sales Office
233 South Hillview Drive
Milpitas, CA95035
tel: (408) 934-7500 faX: (408) 935-7600

Sipex Corporation reserves the right to make changes to any products described herein. Sipex does not assume any liability arising out of the application or use of any product or circuit described herein; neither does it convey any license under its patent rights nor the rights of others.

Nov29-06 RevB ANI1: 1.8V RS-232 Interface using SP3203E & SP6661 © 2006 Sipex Corporation Page 2