

# XR224xx USB Hubs

Design Guide

# **Revision History**

Document No.	Release Date	Change Description
203DGR00	4/20/20	Initial release.

# **Table of Contents**

Introduction	1
Reference Documentation	1
Pin Groups	1
Design and Layout Recommendations	2

## **List of Tables**

Fable 1: USB Upstream Port	2
Fable 2: USB Downstream Ports	
Fable 3: USB Hub "Special Handling" Device Pins	
Fable 4: Voltage Rails	
Fable 5: General PCB Layout	

### Introduction

The XR224xx Design Guide a helpful checklist of schematic design and PCB layout tips to aid in applying a XR224xx USB Hub to your PCB design. The XR224xx Family are USB 2.0 4-port and 7-port hub controllers. The XR22404 4-port hub can be configured for downstream device charging and is compatible with Battery Charging specification revision 1.1/1.2.

Please refer to the respective XR224xx Data Sheet for more information.

### Reference Documentation

XR22404 Data Sheet

XR22414 Data Sheet

XR22417 Data Sheet

Visit www.maxlinear.com to obtain copies of these documents.

### Pin Groups

The tables below are arranged by the following pin groups:

- USB Upstream Port
- USB Downstream Ports
- USB Hub other "Special Handling" Device Pins
- Voltage Rails
- General PCB Layout

### **Design and Layout Recommendations**

#### **Table 1: USB Upstream Port**

#### Schematic Design Recommendations

Ensure there are no external components on **USBD+** / **USBD-** unless tested in compliance with the USB 2.0 spec. For example, no series resistance, inductance or capacitance. No shunt capacitance. Exceptions are ESD protection diodes, EMI filters that have demonstrated compliance with USB 2.0 high speed signaling.

#### **Layout Recommendations**

**USBD+** / **USBD-** are high speed USB signaling at 480MHz. Ensure 90Ω differential impedance.

**USBD+** / **USBD-** should not be routed over a split reference plane.

USBD+ / USBD- should be length matched, ideally to within ±20 mils.

USBD+ / USBD- should have no greater than 2 vias.

USBD+ / USBD- should have no stubs on these traces greater than 200 mils, for example to test points.

#### Table 2: USB Downstream Ports

#### **Design and Layout Recommendations**

All downstream ports of the USB hubs may operate at high, full or low speed, depending on the speed of the attached device. All notes regarding the USB upstream port should also be followed by all downstream port USB data signals.

#### Table 3: USB Hub "Special Handling" Device Pins

#### **Schematic Design Recommendations**

Connect **VBUS\_SENSE**, using pin description in the Data Sheet, with voltage divider from USB host VBUS power input. Required for proper operation in self-powered USB designs.

For USB suspend mode power compliance, use the LOW\_PWR# output to power down other devices powered by USB VBUS.

#### **Layout Recommendations**

Connect XTAL pins with short traces isolated from other high frequency nets.

Connect REXT with short trace.

Use power plane, partial power plane or heavy power trace to connect 3V3\_OUT to VCC33 pins when powered by 5V V<sub>CC</sub>.

Use power plane, partial power plane or heavy power trace to connect 1V8\_OUT to VCC18 pins.

#### Table 4: Voltage Rails

#### **Schematic Design Recommendations**

An in-rush current limiting circuit is recommended (refer to XR224xx Evaluation board schematics) to meet USB compliance.

All decoupling capacitors should be implemented without traces to power or ground rails if possible.

#### Bulk decoupling:

USB requires between 1 and 10 $\mu$ F of bulk capacitance on the VBUS power rail from the USB host. We recommend 4.7 $\mu$ F. In general if no in-rush current limiting circuit is used, a tantalum capacitor is recommend except for embedded applications or applications where no external USB cable will be used. For all other voltage rails (including any external  $\nu$ CC supply voltages to the XR224xx device in self-powered mode) a minimum of 10 $\mu$ F of bulk decoupling should be used.

#### High frequency decoupling:

For all designs, a 100nF high frequency decoupling capacitor is recommended on each power pin, located as close as possible to the device power pin.

#### Table 5: General PCB Layout

#### **Layout Recommendations**

A minimum of a 4 layer PCB is critical with 5V or 3.3V power and ground reference planes (2 and 3) and microstrip signal layers (layers 1 and 4).



MaxLinear, Inc. 5966 La Place Court, Suite 100 Carlsbad, CA 92008 760.692.0711 p. 760.444.8598 f.

www.maxlinear.com

The content of this document is furnished for informational use only, is subject to change without notice, and should not be construed as a commitment by MaxLinear, Inc. MaxLinear, Inc. assumes no responsibility or liability for any errors or inaccuracies that may appear in the informational content contained in this guide. Complying with all applicable copyright laws is the responsibility of the user. Without limiting the rights under copyright, no part of this document may be reproduced into, stored in, or introduced into a retrieval system, or transmitted in any form or by any means (electronic, mechanical, photocopying, recording, or otherwise), or for any purpose, without the express written permission of MaxLinear, Inc.

Maxlinear, Inc. does not recommend the use of any of its products in life support applications where the failure or malfunction of the product can reasonably be expected to cause failure of the life support system or to significantly affect its safety or effectiveness. Products are not authorized for use in such applications unless MaxLinear, Inc. receives, in writing, assurances to its satisfaction that: (a) the risk of injury or damage has been minimized; (b) the user assumes all such risks; (c) potential liability of MaxLinear, Inc. is adequately protected under the circumstances.

MaxLinear, Inc. may have patents, patent applications, trademarks, copyrights, or other intellectual property rights covering subject matter in this document. Except as expressly provided in any written license agreement from MaxLinear, Inc., the furnishing of this document does not give you any license to these patents, trademarks, copyrights, or other intellectual property.

MaxLinear, the MaxLinear logo, and any MaxLinear trademarks, MxL, Full-Spectrum Capture, FSC, G.now, AirPHY and the MaxLinear logo are all on the products sold, are all trademarks of MaxLinear, Inc. or one of MaxLinear's subsidiaries in the U.S.A. and other countries. All rights reserved. Other company trademarks and product names appearing herein are the property of their respective owners.

© 2020 MaxLinear, Inc. All rights reserved.